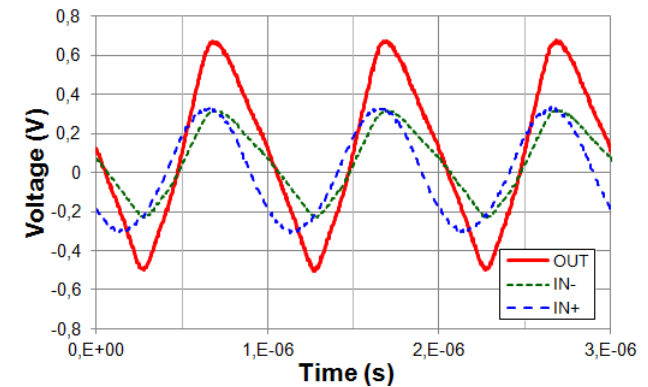


A CASE STUDY TO APPREHEND RF SUSCEPTIBILITY OF OPERATIONAL AMPLIFIERS



A. Boyer^{1,2}, Etienne Sicard¹

¹ INSA Toulouse, University of Toulouse, 31077 Toulouse, France

²LAAS-CNRS, 7 avenue du colonel Roche, 31077 Toulouse, France


www.ic-emc.org

Outlines

- Purpose
- Experimental results
- Failure analysis
- Modeling op-amp susceptibility
- Validation of the model
- Conclusion


Purpose

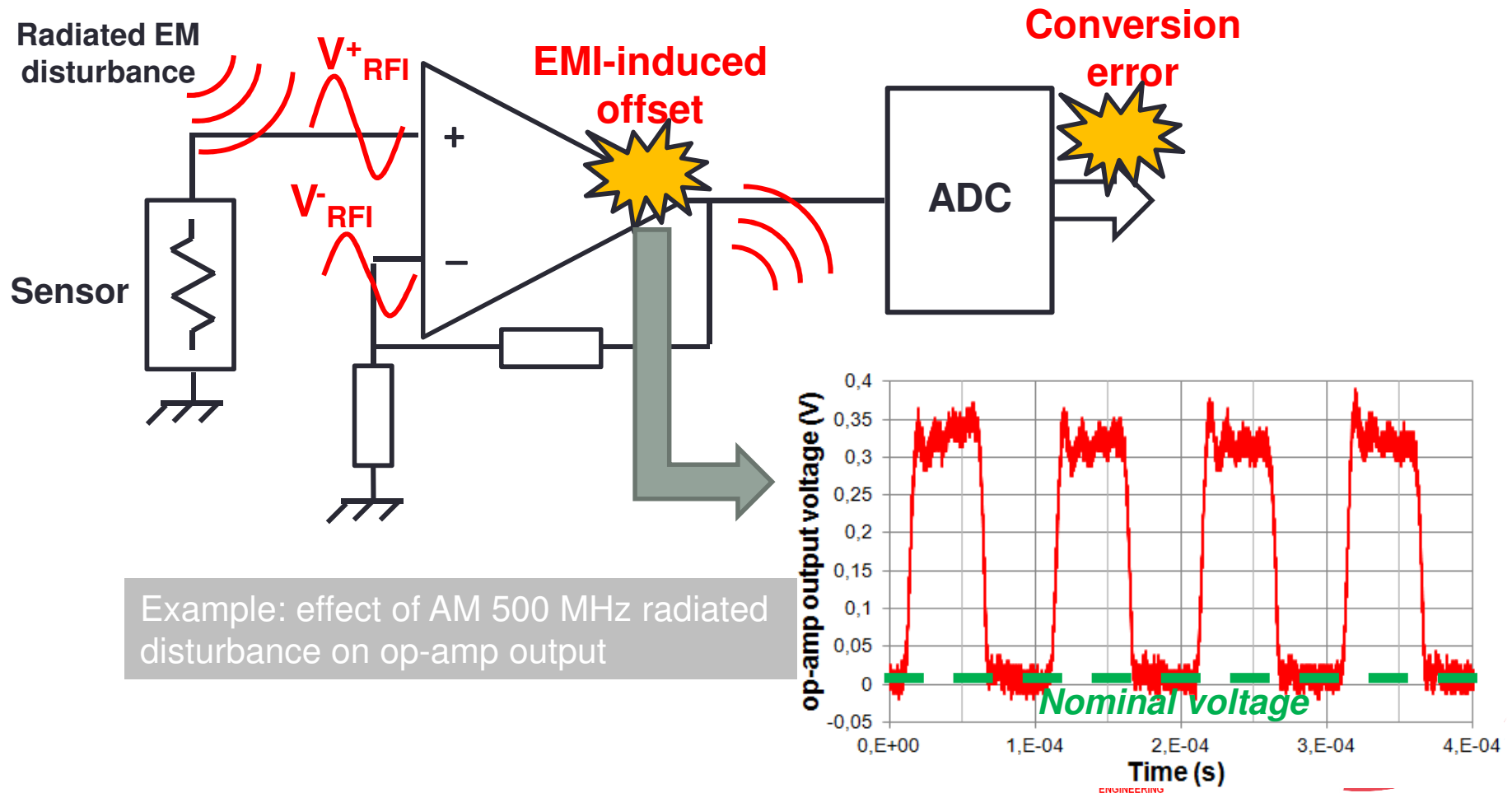- Analog amplifiers **very common** in signal conditioning
- **Very sensitive** to out-of-band electromagnetic disturbance, specifically differential inputs



Purpose

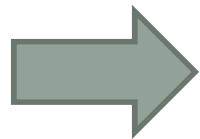- Many researches on **modeling** of the failure mechanisms and **op-amp design improvement**
- Issue still **misunderstood** by most electronic designers
- **No simple models** available to validate their design





- ✓ Dedicated training to clarify this problem (observation by measurement, modeling, evaluation of design guidelines)
- ✓ Based on low-cost demo board and SPICE simulation

- J. G. Tront, J. J. Whalen, C. E. Larson, J. M. Roe, "Computer-Aided Analysis of RFI Effects in Operational Amplifiers", IEEE Trans. on EMC, 21, (4), Nov. 1979
- D. Golzio, S. Graffi, G. Masetti, "New Circuit Modeling of Operational Amplifiers", IEEE Int. Symp on EMC, USA, 1989
- F. Fiori, "A New Nonlinear Model of EMI-Induced Distortion Phenomena in Feedback CMOS Operational Amplifiers", IEEE Trans on EMC, 44, (4), Nov. 2002
- J. M. Redouté, M. Steyaert, EMC of Analog Integrated Circuits, Springer, 2010
- ...

Purpose

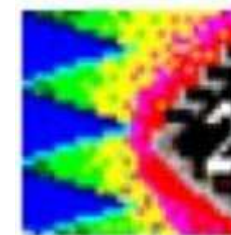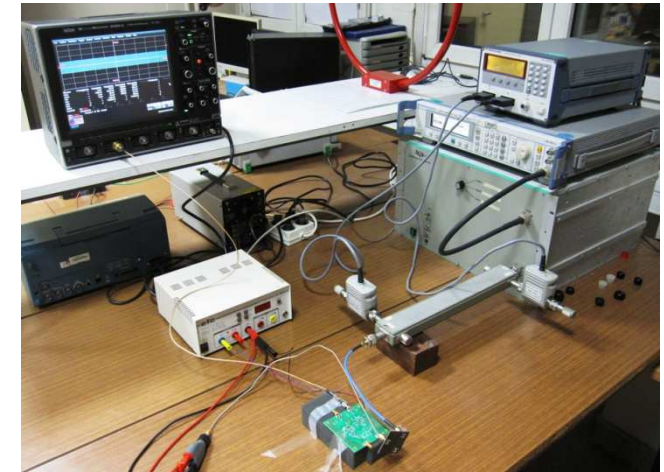- Contents of the training:
 - ✓ Illustration on a real **case-study**
 - ✓ Presentation of **conducted immunity test-bench**
 - ✓ Analysis of the **failure** mechanisms
 - ✓ EMI-hardened vs. non-hardened op-amp
 - ✓ Building of **susceptibility models** of op-amp
 - ✓ **Simulation of DPI** tests on op-amp
 - ✓ Evaluation of **design guidelines** for improved **immunity**



www.ic-emc.org

Presentation of the experiments

- Two comparable amplifiers from www.ti.com

LMV651  ACTIVE

In English ▾

Alert me

Single 12 MHz, low voltage, low power amplifier



DATASHEET

[LMV65x 12-MHz, Low Voltage, Low Power Amplifiers datasheet \(Rev. K\)](#)

 View now  Download

LMV851  ACTIVE

In English ▾

Alert me

Single 8 MHz Low Power CMOS, EMI Hardened Operational Amplifier



DATASHEET

[LMV851/LMV852/LMV854 8 MHz Low Power CMOS, EMI Hardened Operational Amplifiers datasheet \(Rev. A\)](#)

 Download


Presentation of the experiments

- TI's universal op amp evaluation board 551012875
- Comparison of conducted immunity on V+ and Vout

EMI Hardened



Characteristics	LMV651	LMV861
Power supply	+/- 2.5 V	+/- 2.5 V
Static gain	93 dB	110 dB
GBW product	12 MHz	30 MHz
Slew rate +/- (not specified by datasheet)	3.6 / -2.2 V/ μ s	21.2 / -24.2 V/ μ s
Max. input offset voltage	1.5 mV	1 mV
CMRR	100 dB	93 dB
PSRR	95 dB	93 dB
EMIRR	Not defined	70 - 110 dB (400-2400 MHz)


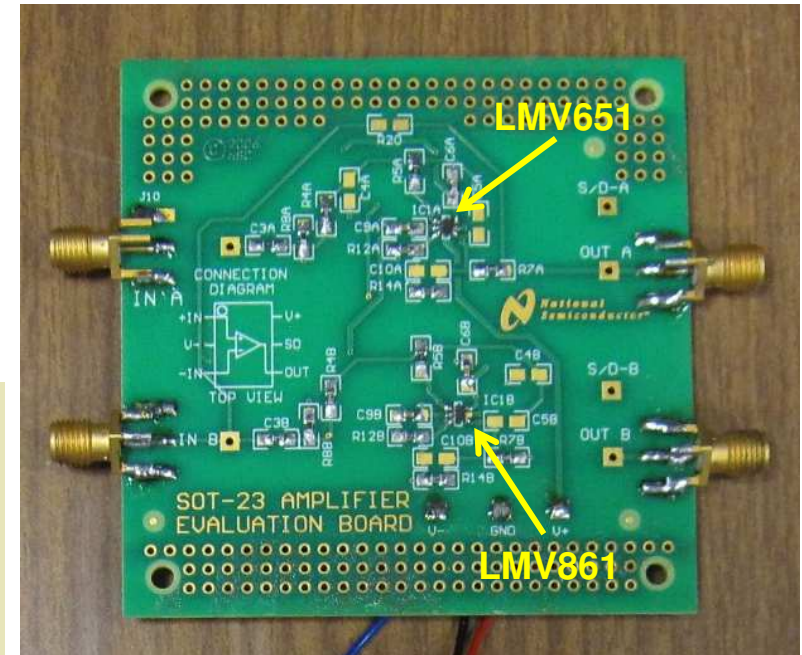


$$EMIRR = \frac{\Delta V_{pp}}{V_{offset_out}}$$

Applied disturbance amplitude
Induced output offset


Presentation of the experiments

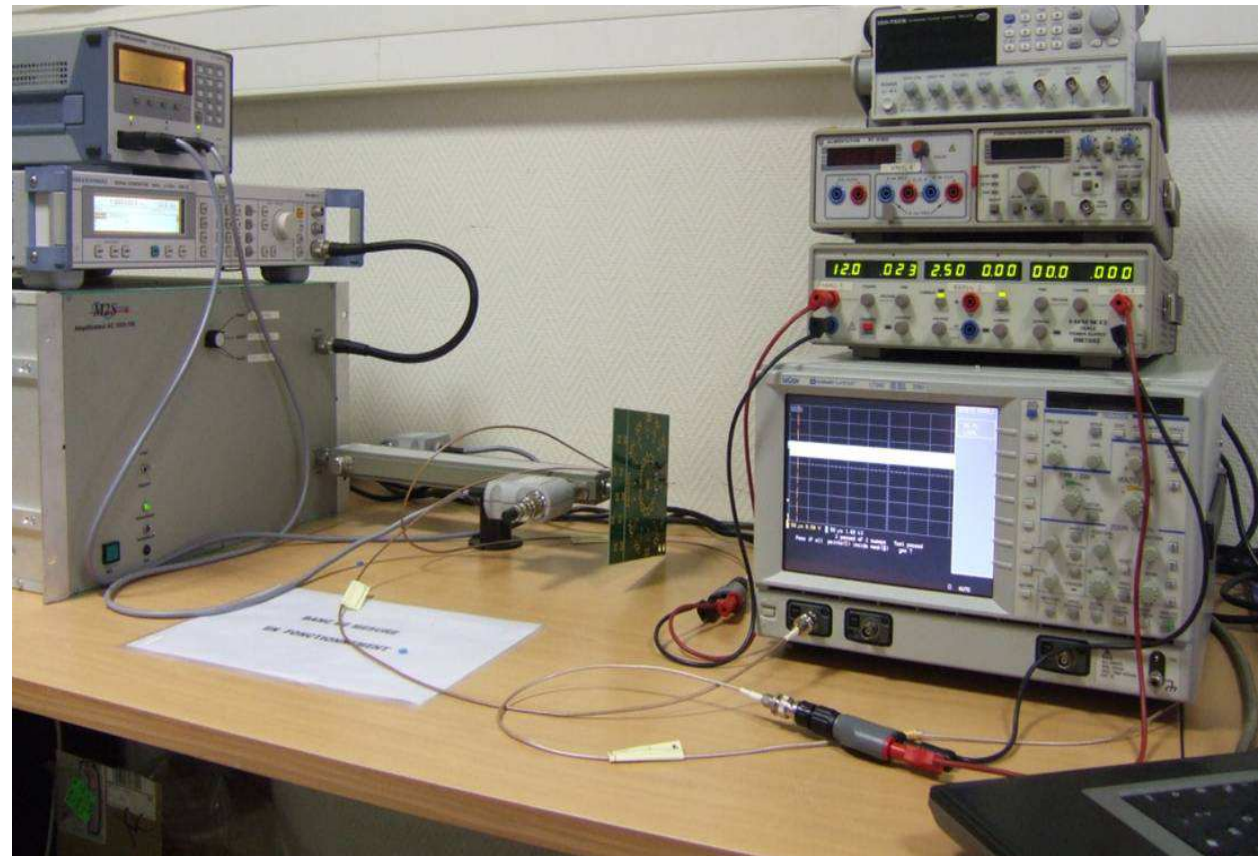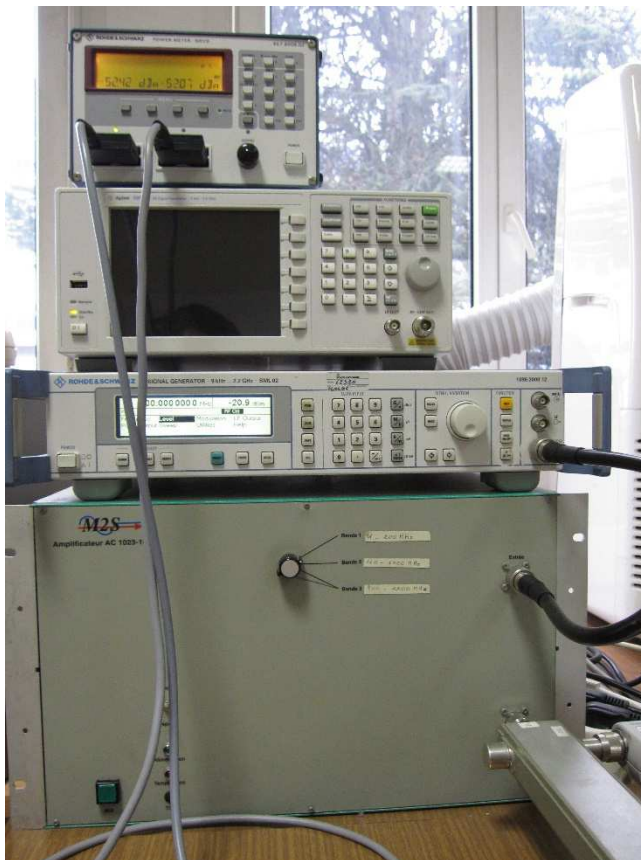- DPI test bench at INSA
- Very **close to IEC 62132-4** Direct Power Injection tests from 1 MHz to 1 GHz
- Forward power = **25 dBm** (0,3W)





Experimental results

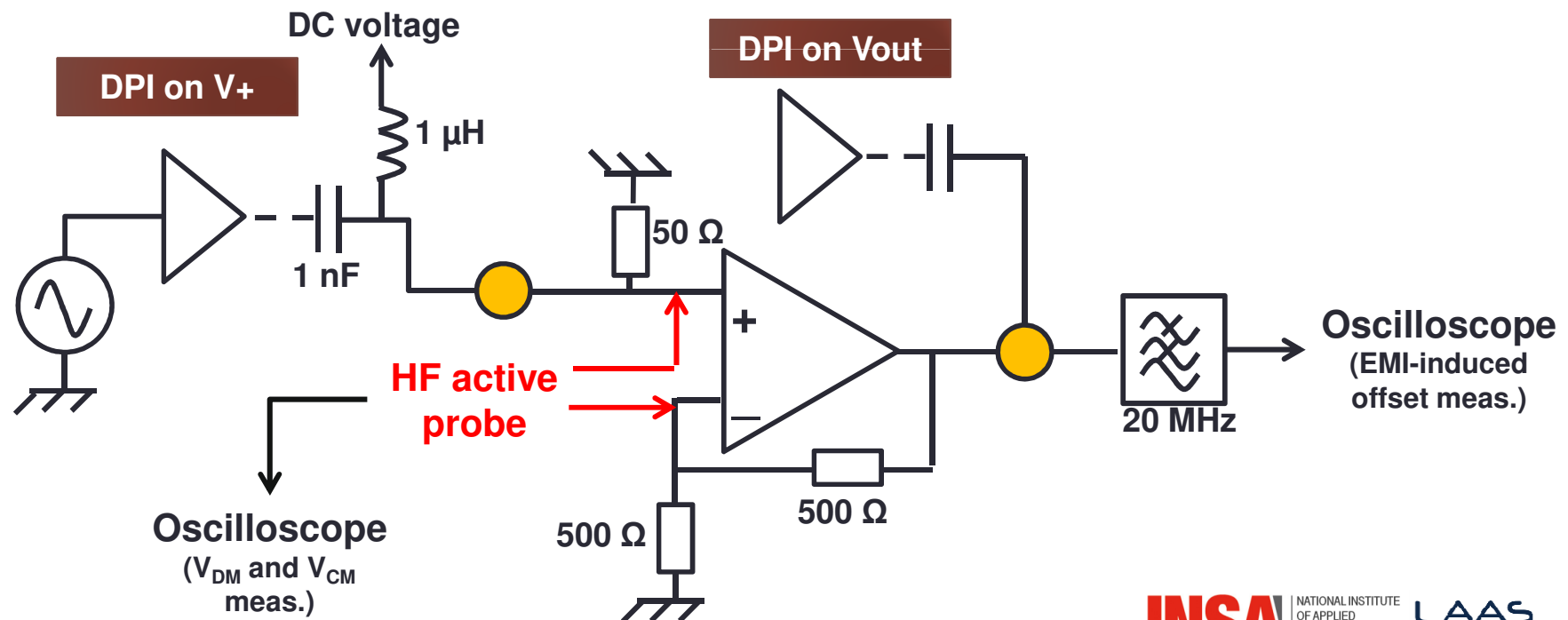- Op-amp mounted on **non-inverting amplifier** configuration (gain x2)
- Injection on non-inverting **input V_+ and V_{out}** .
- Failure criterion: +/-100 mV output offset



Experimental results

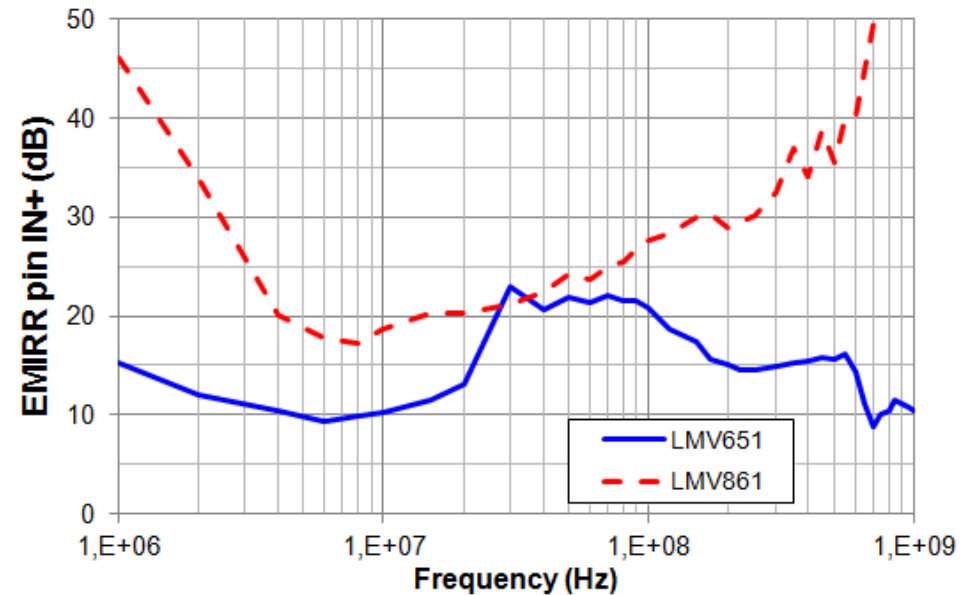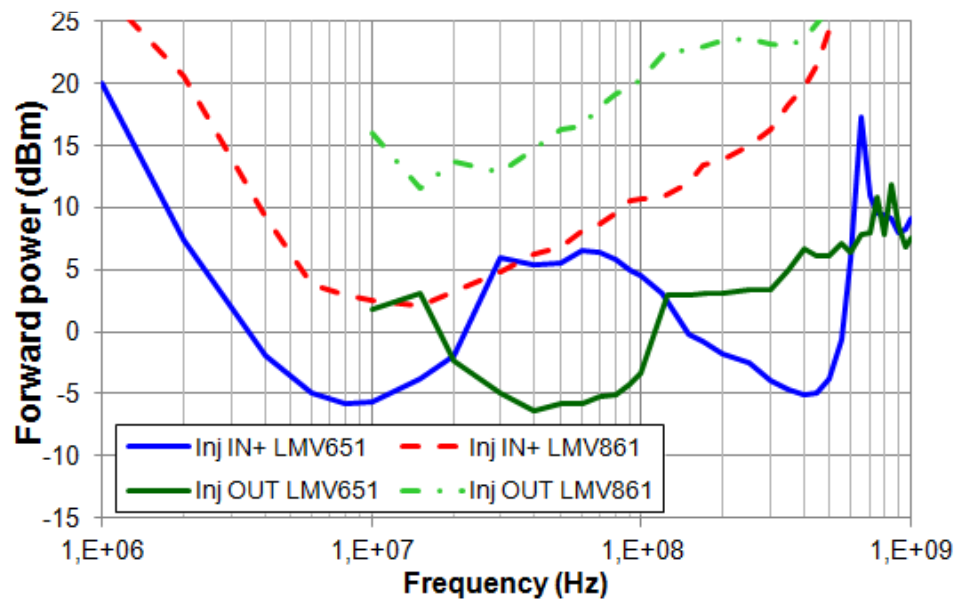- **Susceptibility level** and EMIRR measurements on IN+ and Vout
- EMI-hardened version is the **most robust**, except between 25 and 60 MHz.
- Different **types of failures** appear depending on frequency




Failure analysis

- Low-frequency DPI failure: slew-rate asymmetry

LMV651


$SR_+ > SR_-$ (3.6 / -2.2 V/ μ s)

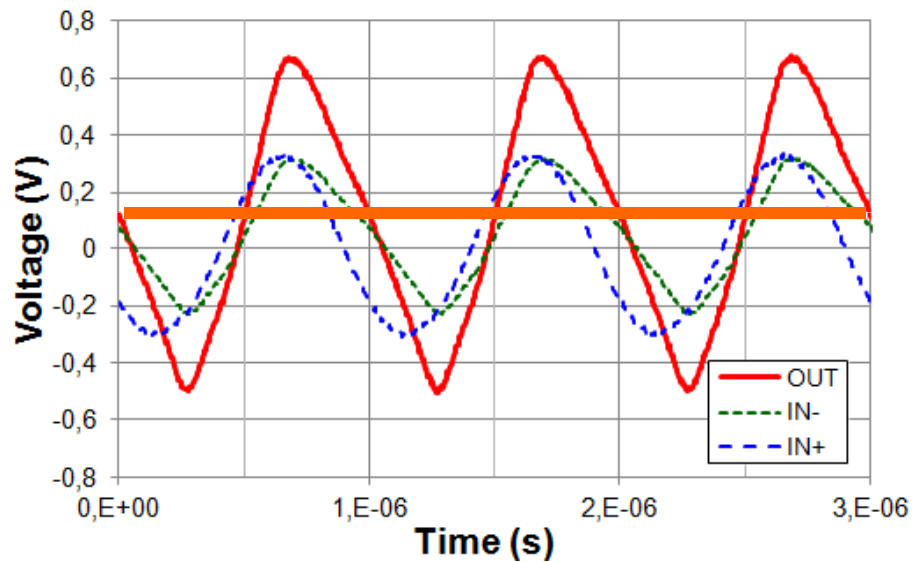

Positive offset

LMV861

$SR_+ < SR_-$ (21.2 / -24.2 V/ μ s)

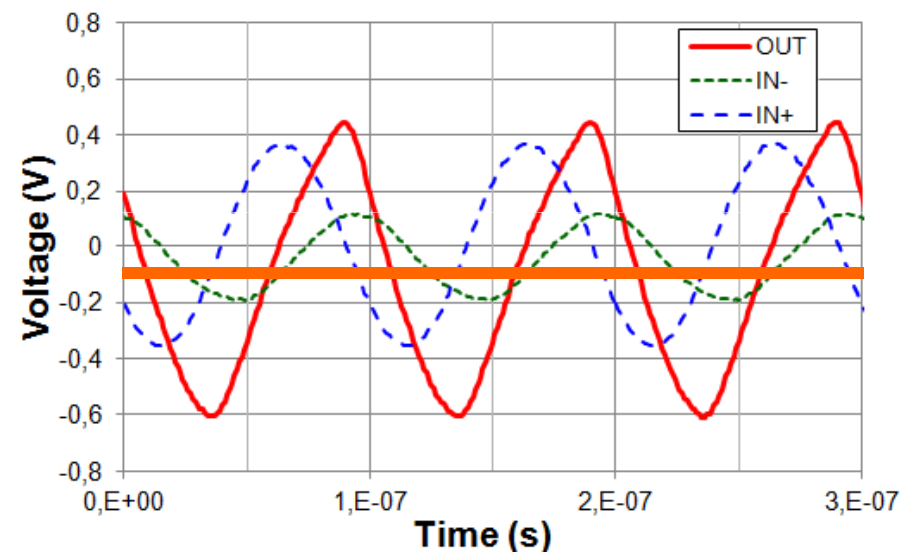


Negative offset

Failure analysis

- For both op-amps, three failure mechanisms are observed:

- Up to some tens of MHz : **positive offset, quasi-linear increase** with EM disturbance amplitude (**slew rate asymmetry**)
- Above some tens of MHz : **negative offset, rapid increase** with EM disturbance amplitude (**weak distortion**)
- High frequency and large disturbance level : **saturation of the output (asymmetrical cut-off)**

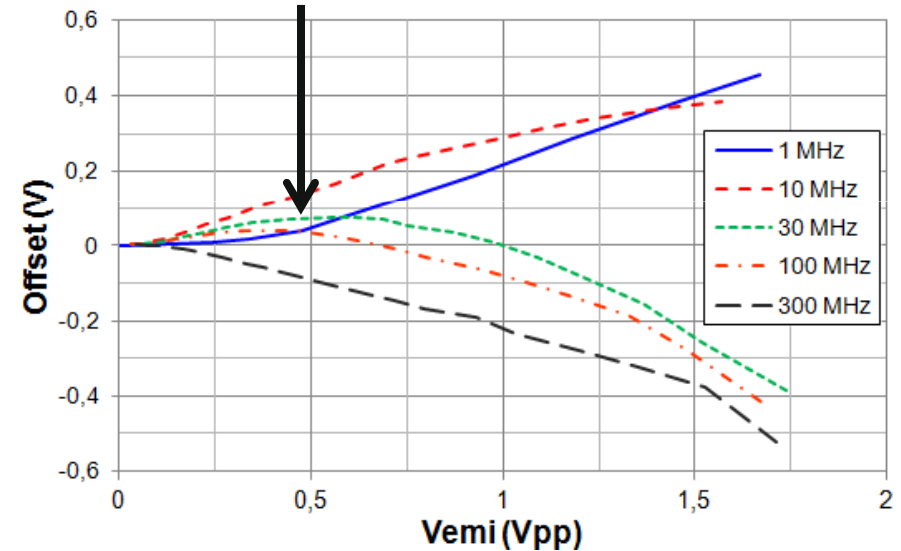
Compensation of failure mode 1 by failure mode 2



Evolution of EMI-induced offset vs. disturbance amplitude and frequency

Failure analysis

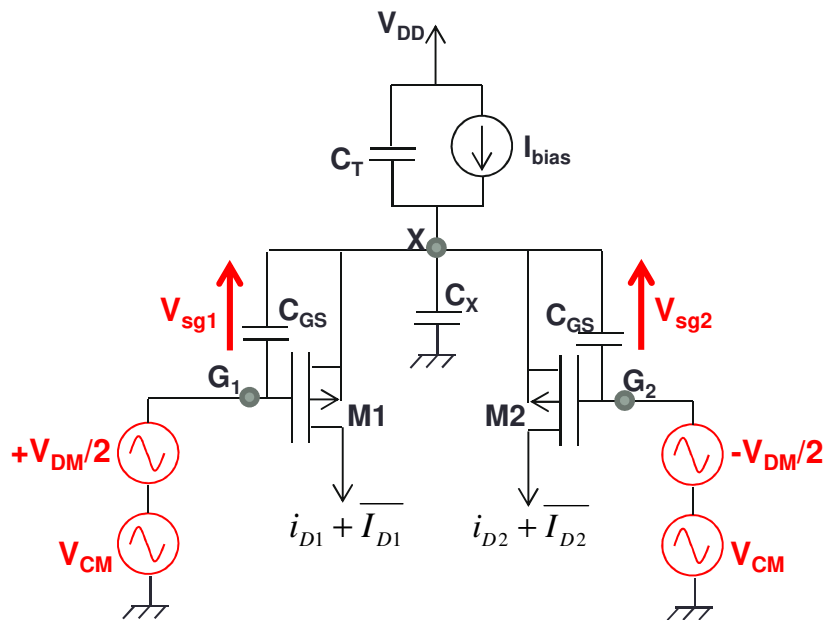- High-frequency DPI failure: weak distortion brought by input differential pair



- ✓ Non linear behavior of MOS transistor leads to rectification of induced RF current
- ✓ Generation of drain current offsets (I_{D1} and I_{D2})
- ✓ Induced drain current imbalance ΔI_D :

$$\Delta I_D = \overline{I_{D1}} - \overline{I_{D2}} = \frac{\mu_P C_{ox}}{2} \frac{W}{L} \left(\overline{v_{sg1}^2} - \overline{v_{sg2}^2} \right)$$

- ✓ Drain current imbalance if:
 - Diff. mode voltage $V_{DM} \neq 0$
 - Common-mode voltage $V_{CM} \neq 0$
- ✓ Theoretical EMI-induced input-related voltage offset:

$$V_{off_in} = \frac{-1}{2|V_{sg} - V_T|} |V_{DM} V_{CM} H_{CM}| \cos(\phi + \arg(H_{CM}))$$

With:
$$H_{CM} = \frac{V_{sg}}{V_{CM}} = \frac{j\omega(C_T + C_X)}{j\omega(2C_{gs} + C_T + C_X) + 2g}$$

and ϕ is the phase between V_{DM} and V_{CM}

High-pass behavior

Modeling op-amp susceptibility

- **No susceptibility models** provided by manufacturers (even the slew rate asymmetry is not given)
- Failure mechanisms are based on **complex mechanisms**, whose accurate modeling requires unknown information for end-users



Propose a simplified equivalent electrical SPICE-based model built from measurement results (no extra measurement and rapid modeling process)




Susceptibility simulation made with IC-EMC freeware

Modeling op-amp susceptibility

- Proposed equivalent **model** for **slew rate asymmetry** and weak distortion effects:

1. Slew rate asymmetry




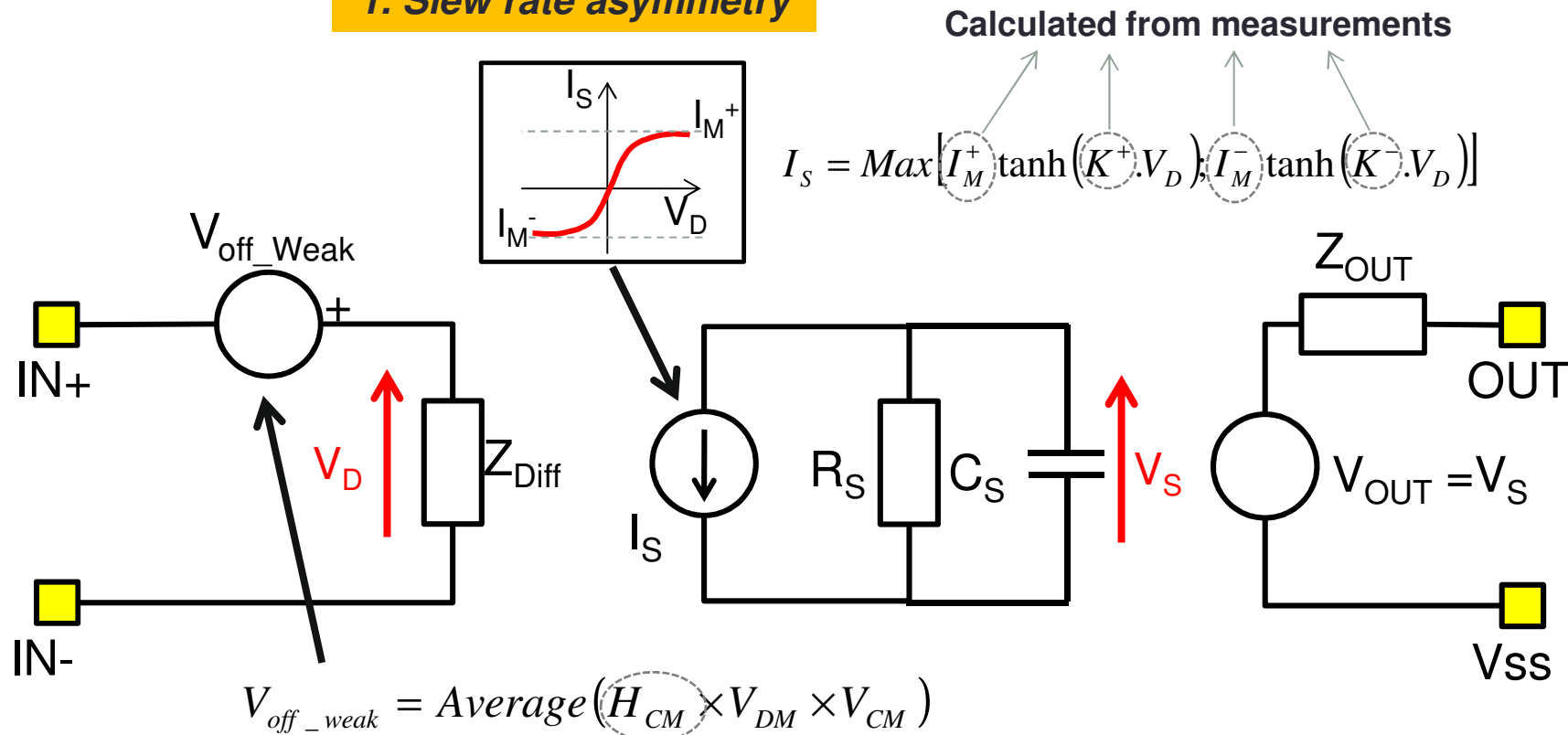


2. Weak distortion

Modeling op-amp susceptibility



- IC-EMC, a tool for simulating emission & **susceptibility of integrated circuits**
 - A schematic editor
 - An interface to WinSpice
 - A post-processor to compare simulated with measured spectrum
 - Freeware, online www.ic-emc.org
 - 250 pp documentation, 15 case studies

Key tools

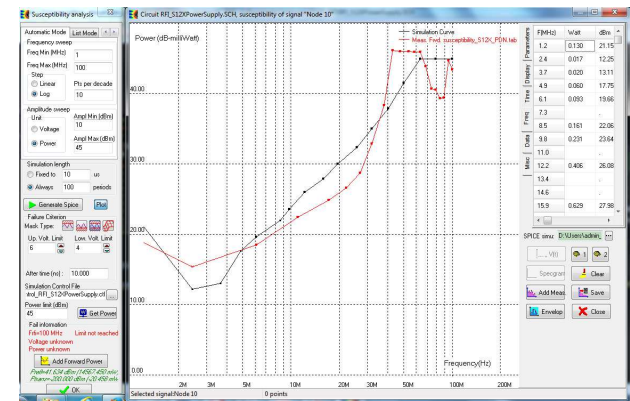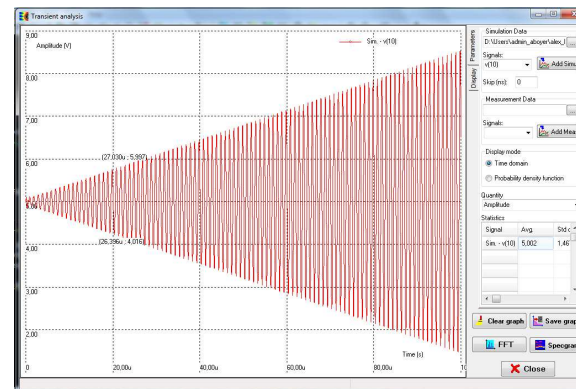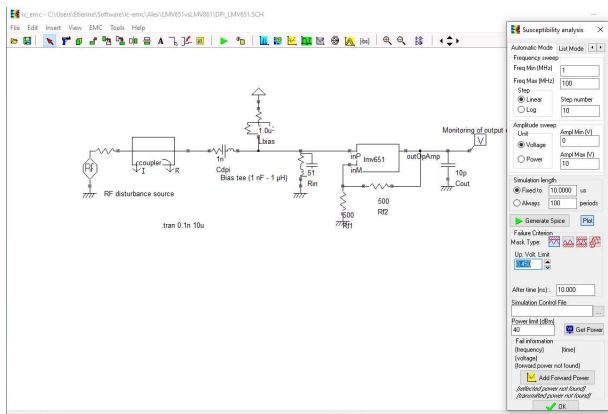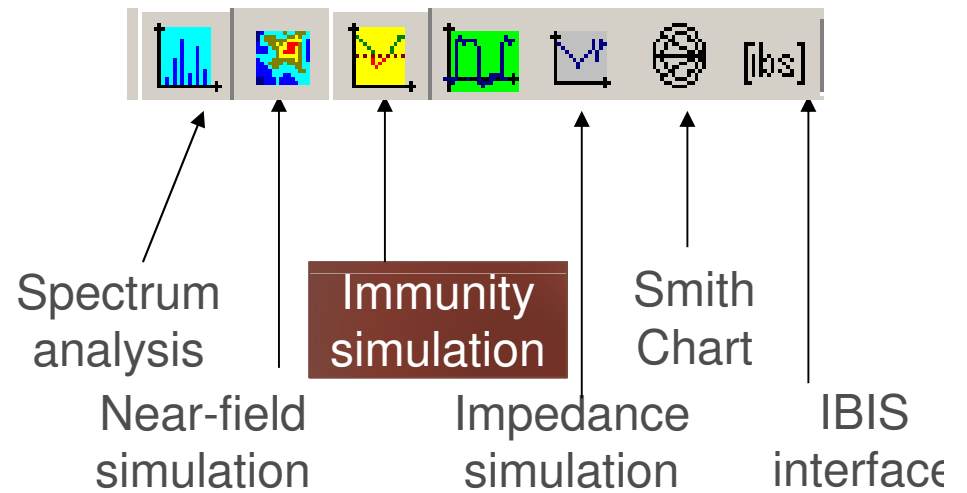

Modeling op-amp susceptibility

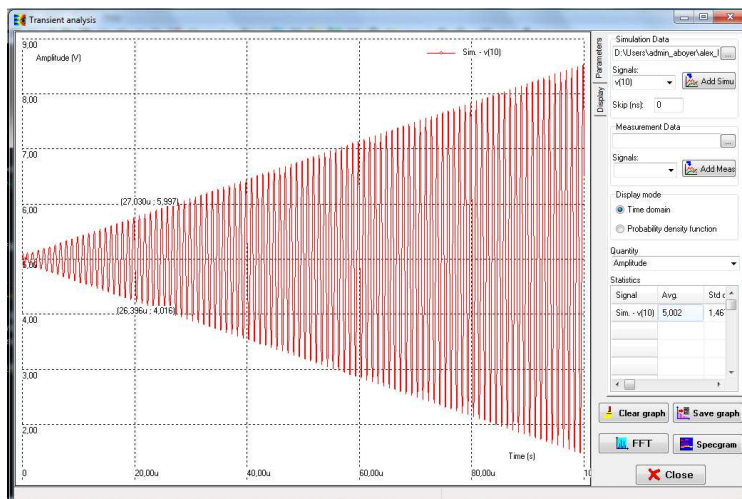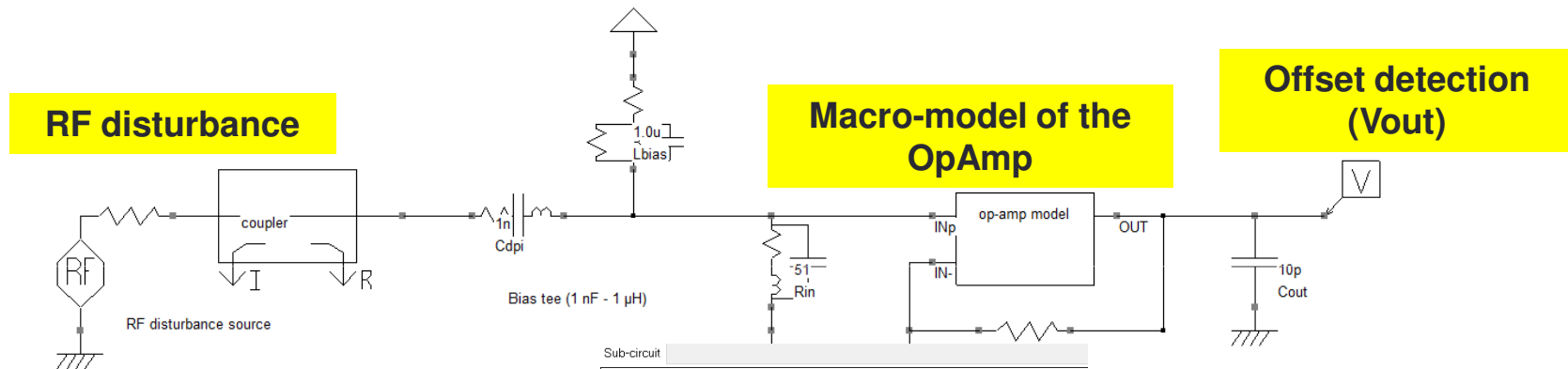- Op-Amp **macro model** described using SPICE “E” elements (any formula)
- DPI simulation in IC-EMC using RF disturbance & coupler
- Iterative simulations with **varying frequencies** (10 per decade)



Sub-circuit



```
* Subcircuit terminals:
* inP -> node number 1
* inM -> node number 2
* outOpAmp -> node number 3
.subckt Imv651 inP inM outOpAmp
* Subcircuit created 24/04/2019 11:29:22
Edm ndm 0 VALUE = V(inP)-V(inM)
Ecm ncm 0 VALUE = (V(inP)+V(inM))/2
Ehcm nhcm 0 ncm 0 -2.75
Chcm nhcm hcm 127p
Rihcm hcm 0 50
Eprod nprod 0 VALUE = V(ndm,0)*V(hcm,0)
*Low pass filter with cut-off frequency = 159 kHz
Rfilt nprod nprod_filt 1k
Cfilt nprod_filt 0 1n
Eis 1 inP_nprod_filt 0 1
*Decomment line below to remove weak distortion effect
*Eis2 1 inP VALUE = 0
*INPUT R
```

```
Edm ndm 0 VALUE = V(inP_f)-V(inM_f)
Ecm ncm 0 VALUE = (V(inP_f)+V(inM_f))/2
E1 n11 0 VALUE = 964e-6*TANH(9.18*V(1,inM_f))
E2 n22 0 0.002 VALUE = 1099e-6*TANH(8.06*V(1,inM_f))
```

```
Rout 80 outOpAmp 3
.ends
```

Validation of the models

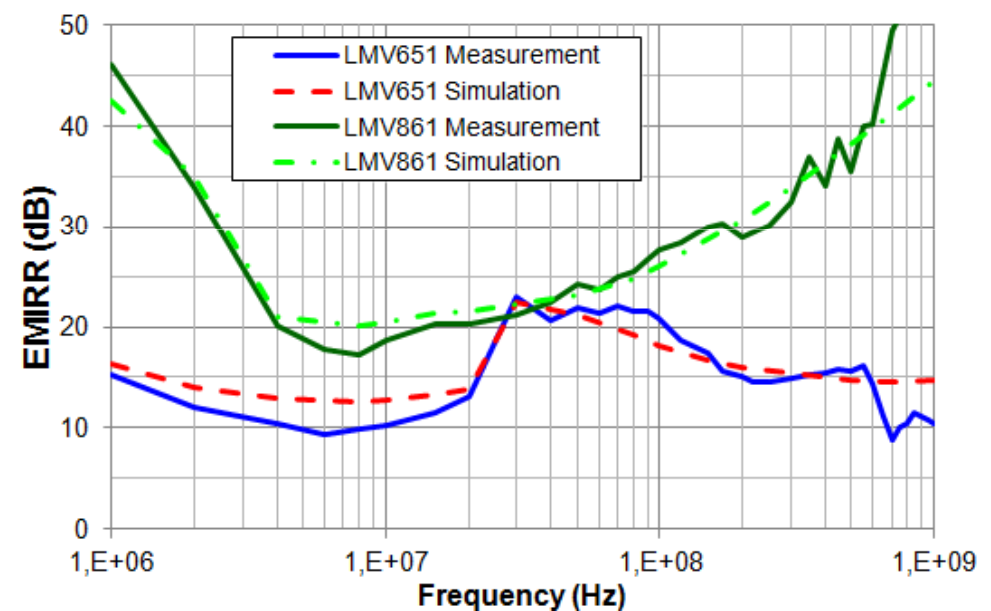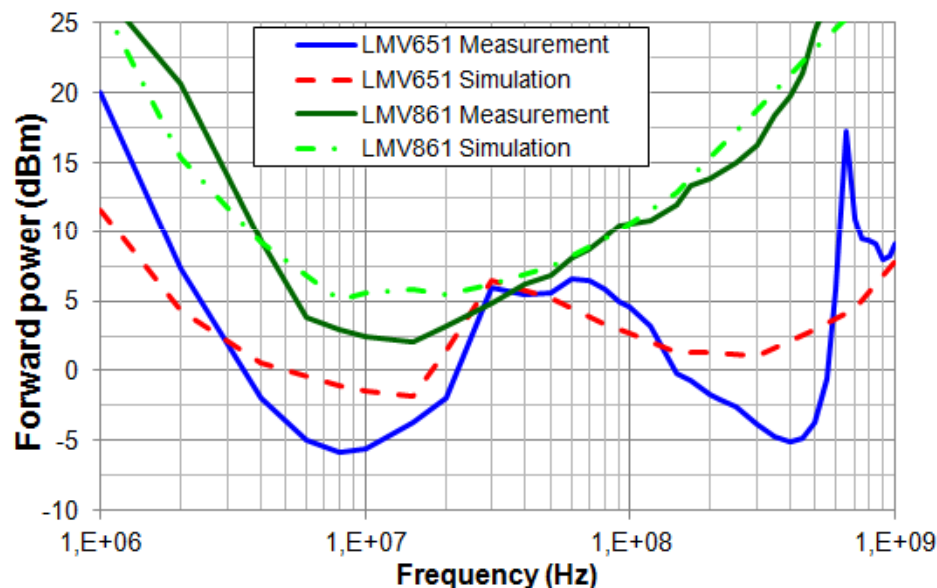
- Comparison between **measurements and simulations** of LMV651 and LMV861 DPI level and EMIRR (non-inverter configuration).
- Injection on non-inverting input



- Quite **good agreement** between 10 and 500 MHz.
- Loss of accuracy** around 10 MHz: limitation of slew rate model
- Loss of accuracy **above 500 MHz**: lack of models of coupling between pins

Validation of the models

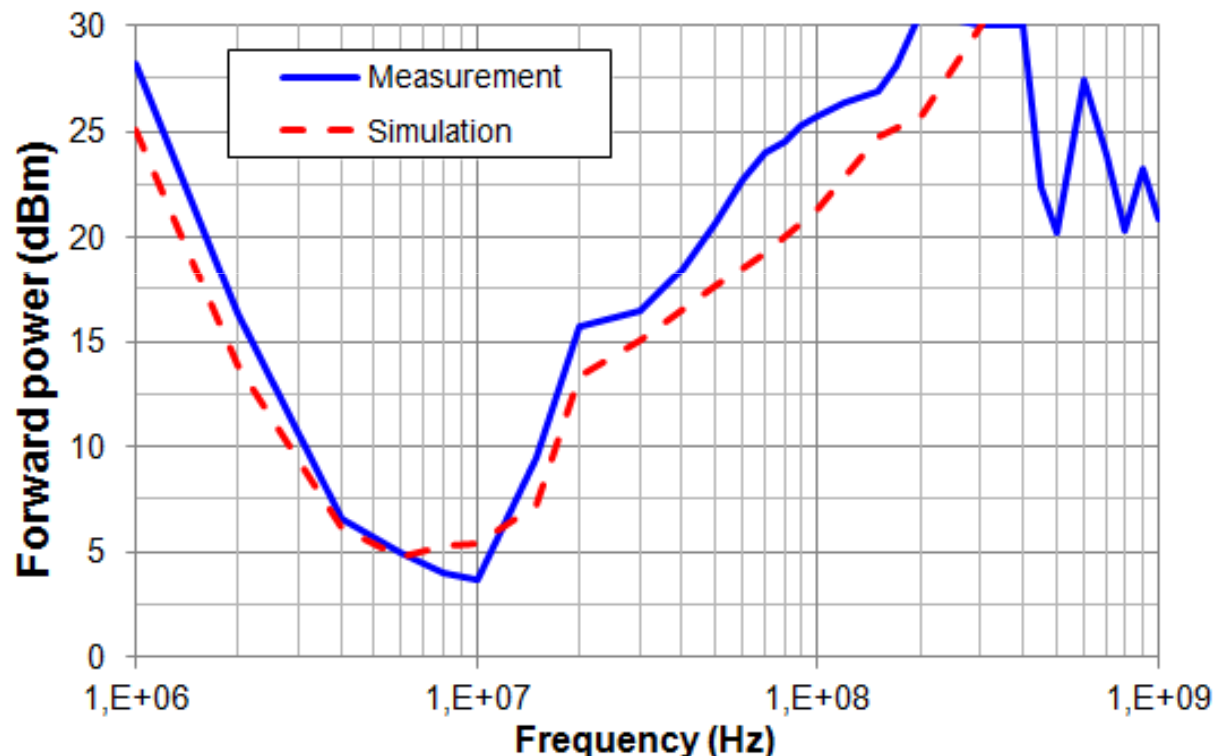
- DPI test in another configuration: voltage follower and **additional external low-pass filter** on non-inverting input pin (LMV651)



- **Good agreement** up to 400 MHz
- Above 400 MHz: limitation of the model

Training scenario & feedback

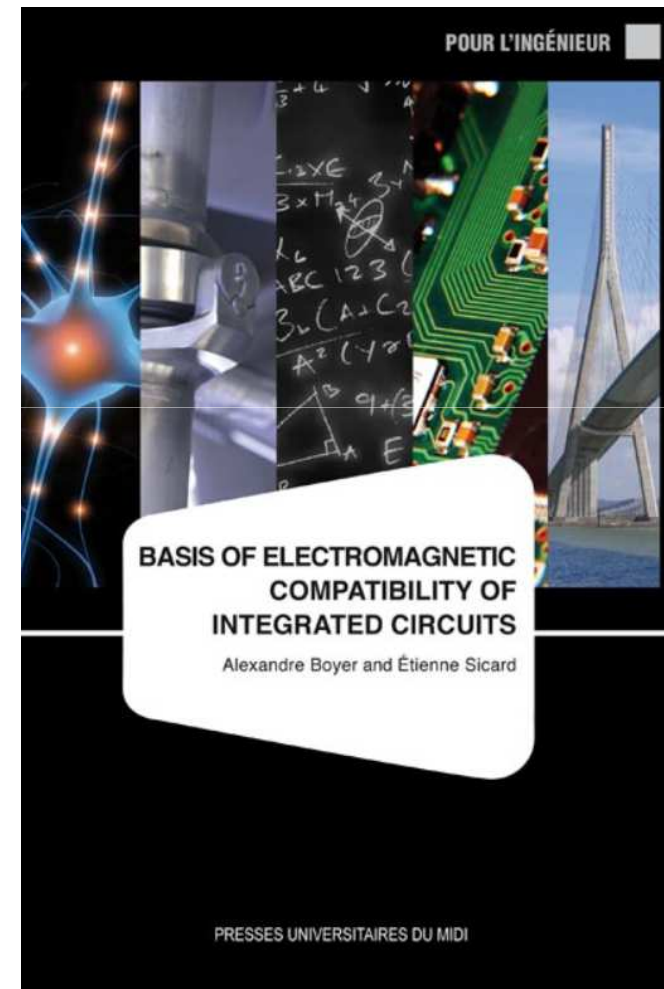- 2-hours measurement :
 - **Discovery** of injection test bench
 - Single-frequency DPI injection to **highlight failure** modes
 - Comparison between **standard & EMI-hardened** OpAmps
- 2-hours simulation;
 - Simulation of DPI test bench on a **resistive load**
 - Simulation of DPI test bench on a **OpAmp model**
- **Positive feedback** from attendees (90% satisfied/100 students)



Conclusion

- A practical training dedicated to the **susceptibility of op-amps** to electromagnetic disturbances:
 - Illustration of typical failure mechanisms
 - Building a simple equivalent electrical model
 - Test different EMI reduction techniques (EMI-robust op-amp, filtering)
- The **simple** op-amp equivalent **model** provides **acceptable prediction** results for op-amp end-users to anticipate EMI issues up to 500 MHz.

THANK YOU FOR YOUR ATTENTION

alexandre.boyer@insa-toulouse.fr

www.ic-emc.org